

**MS FACULTY OF ENGINEERING AND ARCHITECTURE
AMERICAN UNIVERSITY OF BEIRUT**

MIDTERM - PREVIOUS

DIGITAL SYTEMS DESIGN (EECE320)

NAME: _____

ID: _____

CLOSED BOOK (90 MINUTES)

CALCULATORS ARE NOT ALLOWED .

PROVIDE YOUR ANSWERS IN THE SPACE PROVIDED ON THE QUESTION SHEET.

THE SCRATCH BOOKLET WILL NOT BE CONSIDERED IN GRADING.

BE AS NEAT AND CLEAR AS POSSIBLE.

GOOD LUCK!

Problem	Total Points	Earned Points
1	20	
2	4	
3	6	
4	8	
5	8	
6	8	
7	8	
8	8	
9	6	
10	12	
11	12	
Total	100	

Problem 1 (20 points)

a) Convert the following binary number to **Hexadecimal**:

$$100111001011010.101111 = (\rule{10cm}{0.4pt})_{16}$$

b) Convert the following binary number to **Octal**:

$$11101110100.01101 = (\rule{10cm}{0.4pt})_8$$

c) Convert this hexadecimal number, **3D7C**, to **Octal**: ($\rule{10cm}{0.4pt}$)₈

d) Represent the following decimal numbers using **two's complement** with just **enough bits**:

$$+77 = (\rule{10cm}{0.4pt}) \quad -59 = (\rule{10cm}{0.4pt})$$

e) The **10's complement** of the decimal number **9039700** is: $\rule{10cm}{0.4pt}$

f) Just apply DeMorgan to complement the following expression and **DO NOT** simplify it:

$$F = Z + Y'(Z' + W)' + X'Y$$

Answer: $\rule{10cm}{0.4pt}$

g) One solution of the quadratic equation ($x^2 - Bx + 16 = 0$) is $x=2$. Accordingly, the base used is: $\rule{1cm}{0.4pt}$ (Note: **B** is equivalent to 11 decimal)

h) Using 5 bits, $N = 11010$. What is the decimal value of **N** if the representation is:

Sign/Magnitude $\rule{2cm}{0.4pt}$ 2's comp $\rule{2cm}{0.4pt}$

i) The **Decimal** number **864** is represented in **Excess-3** code as:


$\rule{10cm}{0.4pt}$

Problem 2 (4 points)

Given $F(A,B,C) = AB' + A'C$, express F as a product of **MAXTERMS**.

 Problem 3 (6 points)

Write the Boolean expression of the following circuit and **reduce it using Boolean algebra**. The expression should contain only AND, OR and NOT operations.



F = _____

Problem 4 (8 points)

We want to design a circuit with 4 inputs (A,B,C,D) and 1 output that will be set to 1 if the number of “zeros” in the inputs is **equal or greater to 3**. Otherwise, it produces a 0. Complete the K-map and derive a minimum **SOP** expression. Finally, implement this function **using only NAND gates**.

		AB			
CD		00	01	11	10
	00				
	01				
	11				
	10				

SOP of F =

Problem 5 (8 points)

Use the Karnaugh map to obtain a minimum **SOP** expression of the following logic function:

$$F = \Sigma_{ABCD}(2, 3, 5, 6, 13, 14, 15) + \Sigma d(1, 8, 9, 11)$$

F = _____

	AB			
CD \	00	01	11	10
00				
01				
11				
10				

Problem 6 (8 points)

Consider the function: $F = \Sigma_{A,B,C,D}(0, 1, 2, 4, 5, 6, 7, 9, 11, 12, 13, 14)$

a) What are the essential prime implicants of F?

b) What are **ALL** the **OTHER** prime implicants of F?

	AB			
CD \	00	01	11	10
00				
01				
11				
10				

Problem 7 (8 points)

For the following logic expression (F), indicate all the transitions that cause a static hazard in the corresponding two-level AND-OR circuit, and suggest a new expression for a hazard-free circuit that realizes the same logic function.

$$F = W'.X + Y'.Z + W.X.Y.Z + X'.Y.Z'$$


Transitions causing hazards are:

	WX			
YZ \	00	01	11	10
00				
01				
11				
10				

Minimum Hazard-Free F = _____

Problem 8 (8 points)

Implement the function $F = A'C + ABC'$ using a **3-to-Decoder** using additional gates. Then Implement F using a **4-input** multiplexer with controls B and C. (**Remember Shannon**)

 **Problem 9 (6 points)**

A half-adder adds only two bits (A and B, without carry-in) and produces two outputs, the sum (S) and carry (C). Write the expressions of S and C in terms of A and B and then implement the following four functions using **ONLY THREE half adders**. You have to show the inputs that are connected to each half adder and what are the outputs of the adders.

$$D = A \oplus B \oplus C$$

$$E = A'BC + AB'C$$

$$F = ABC' + (A'+B')C$$

$$G = ABC$$

Problem 10 (12 points)

We would like to design a circuit that adds two words (A and B) each with two bits (A_2A_1) and (B_2B_1). We want to design the circuit as one block and not as two full bit adders as we did in class. The circuit will have 4 inputs (A_2, A_1, B_2, B_1) and three outputs that represent the sum (S) and the carry (C) (C, S_2, S_1). Start by completing the truth table below, then fill the corresponding K-maps and finally derive the SOP expressions for C, S_2 and S_1 .

Hint: You can fill out the table by considering any row like:

1	0	1	1
---	---	---	---

As $(10) + (11)$ that is $2+3 = 5 = (101)$

A2	A1	B2	B1	C	S2	S1
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0	0	1	1
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

		A2A1			
		00	01	11	10
B2B1	00				
	01				
	11				
	10				

C

		A2A1			
		00	01	11	10
B2B1	00				
	01				
	11				
	10				

 S_2

		A2A1			
		00	01	11	10
B2B1	00				
	01				
	11				
	10				

 S_1

C = _____

S_2 = _____

S_1 = _____

